

# Status of CDS DMILL Prototype

## History and Goals of the Project:

- CDS prototype was designed by Carl Grace in 1999
- translated into DMILL 0.8 m by J.F. Genat, with LBL support in 2000
- delivered in june 2001 and tested by J.F.Genat and R.Sefri
- proof of feasibility of the integration of a full CCD analog readout
- measurement of some figures of merit of the DMILL radhard process
- check of the integration of the classical CDS circuitry



## Scope of this Presentation:

- results of january 2002 tests<sup>(1)</sup> and triggering of new orientations


<sup>(1)</sup>(J.F.Genat, R.Sefri, A.Secroun et E.B.)

text found at [http://www-lpnhep.in2p3.fr/~barrelet/cds\\_test.pdf](http://www-lpnhep.in2p3.fr/~barrelet/cds_test.pdf)


### CDS IN THE CCD READOUT CHAIN:

 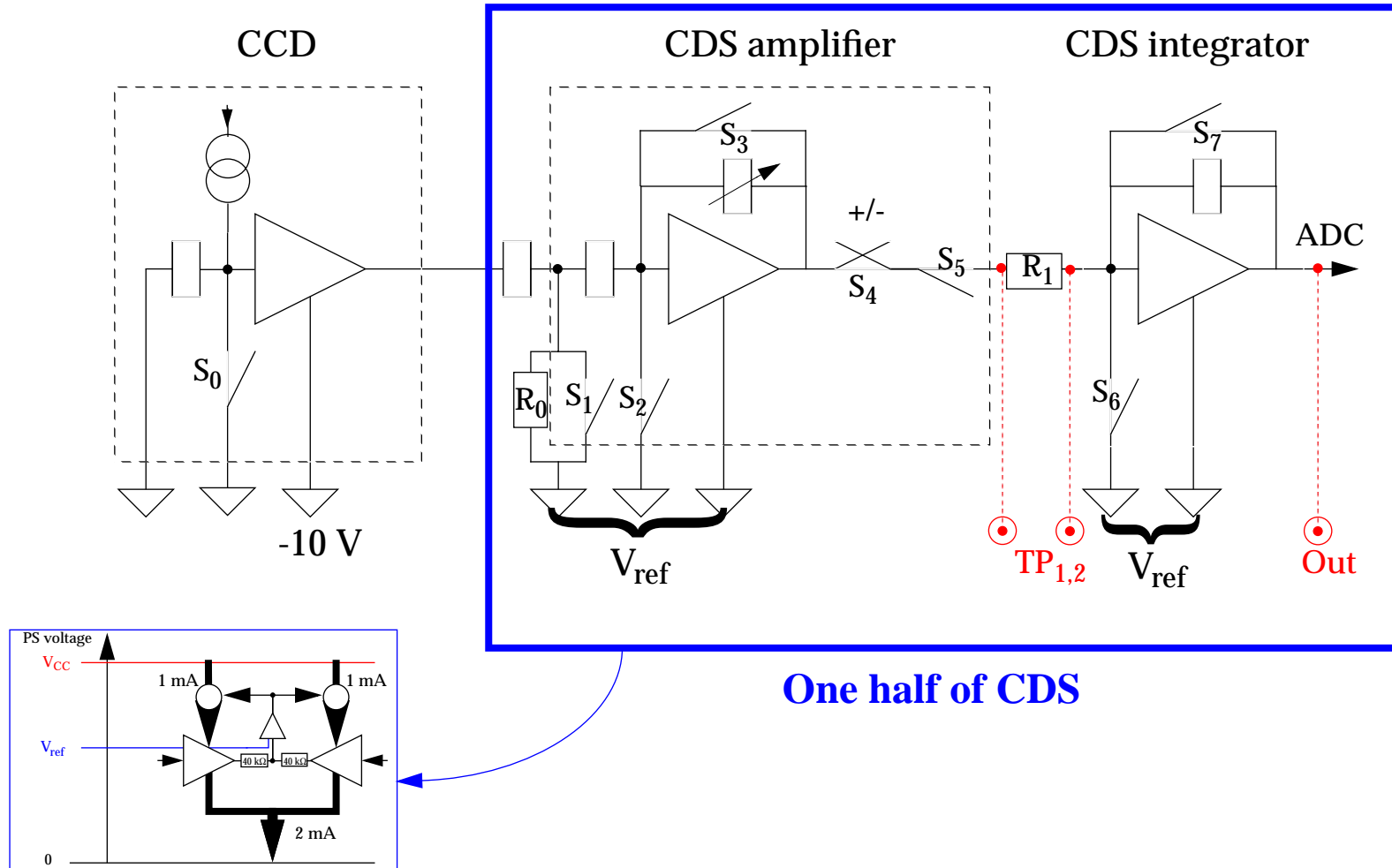


### NEW TEST SETUP ( JANUARY 2002)

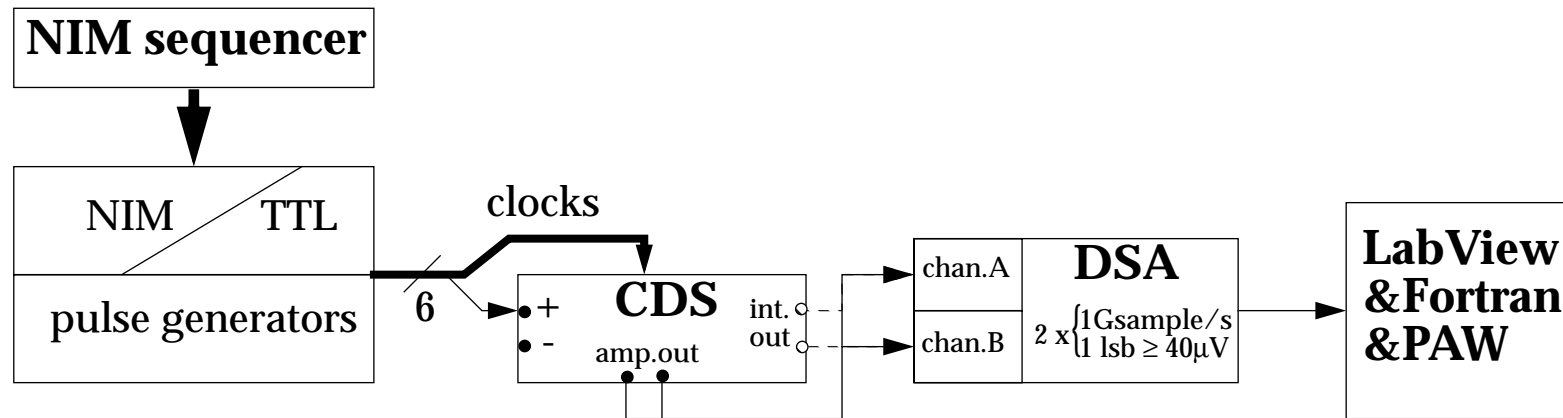

### LINEARITY ~ GAIN ~ RANGE (AMPLIFIER)

 


### AMPLIFIER NOISE 1

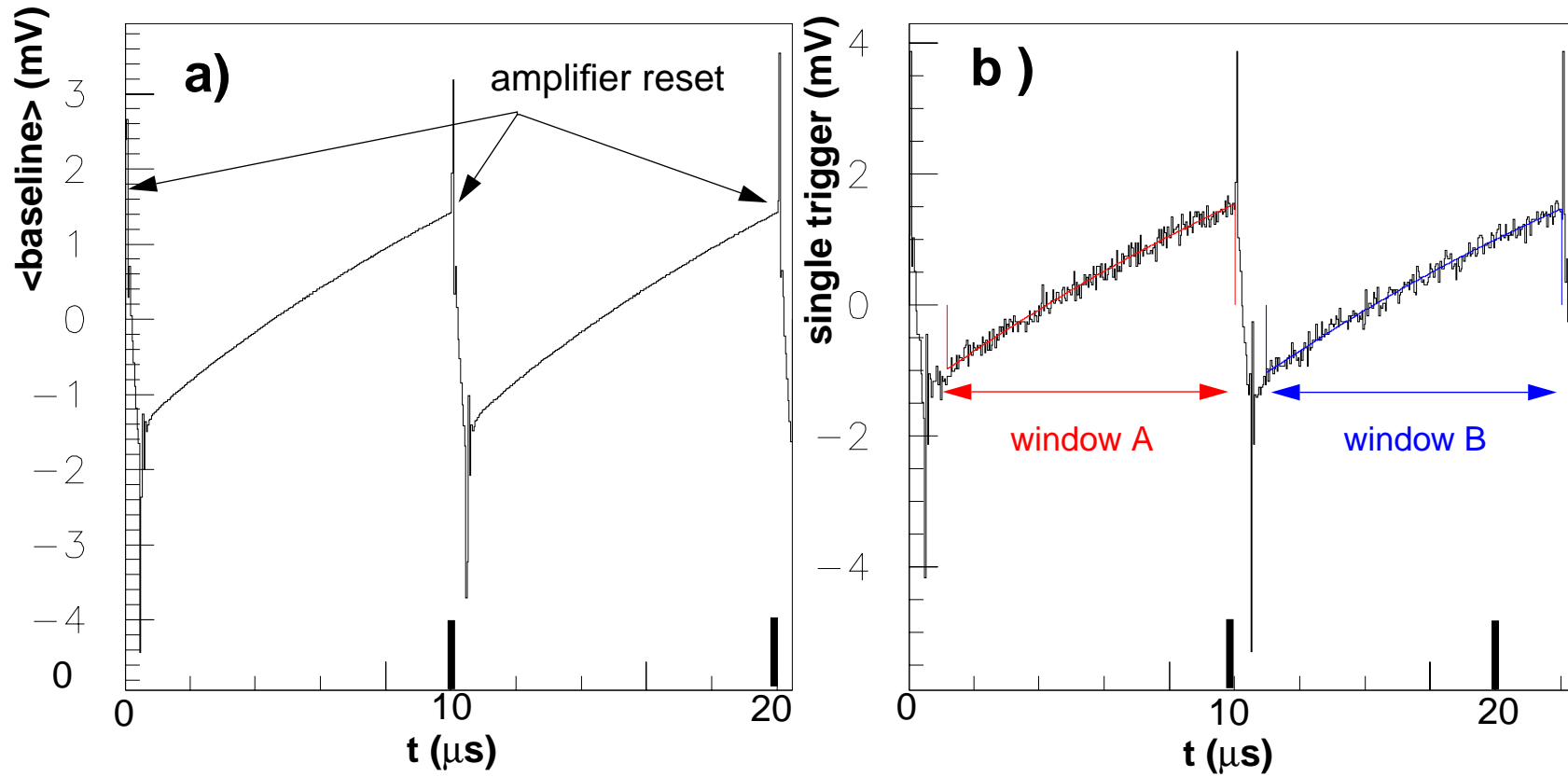


### AMPLIFIER NOISE 2


**nb<sub>sample</sub>**

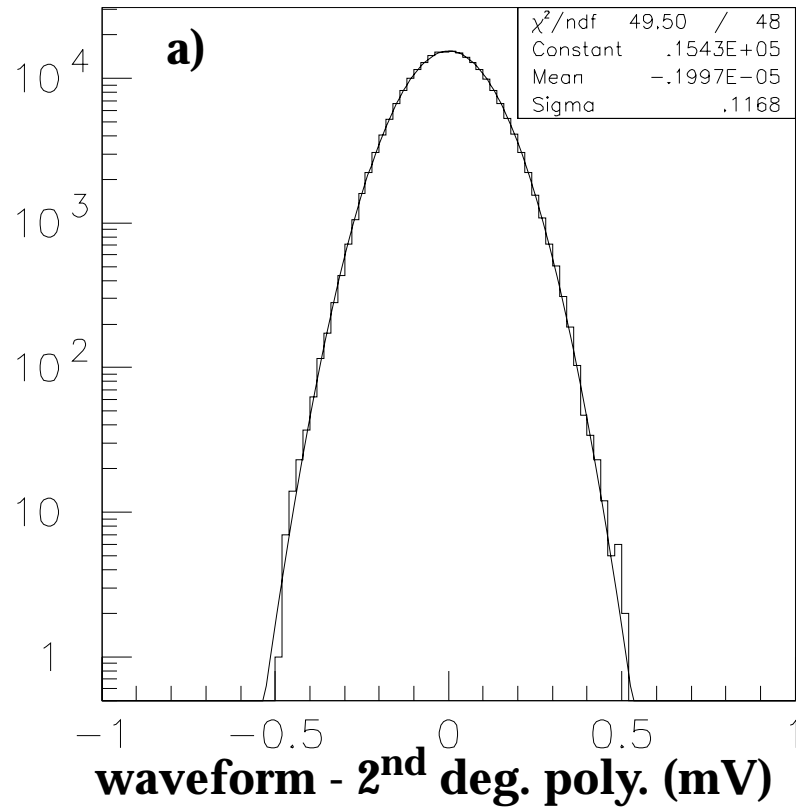

**mV (rms)**

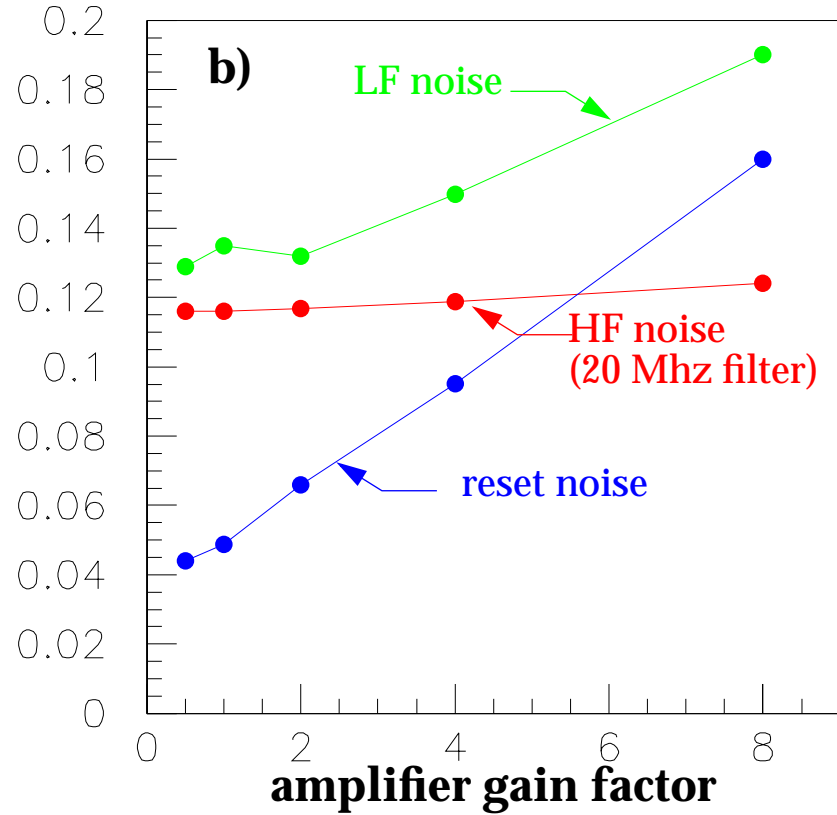


# INTEGRATOR NOISE

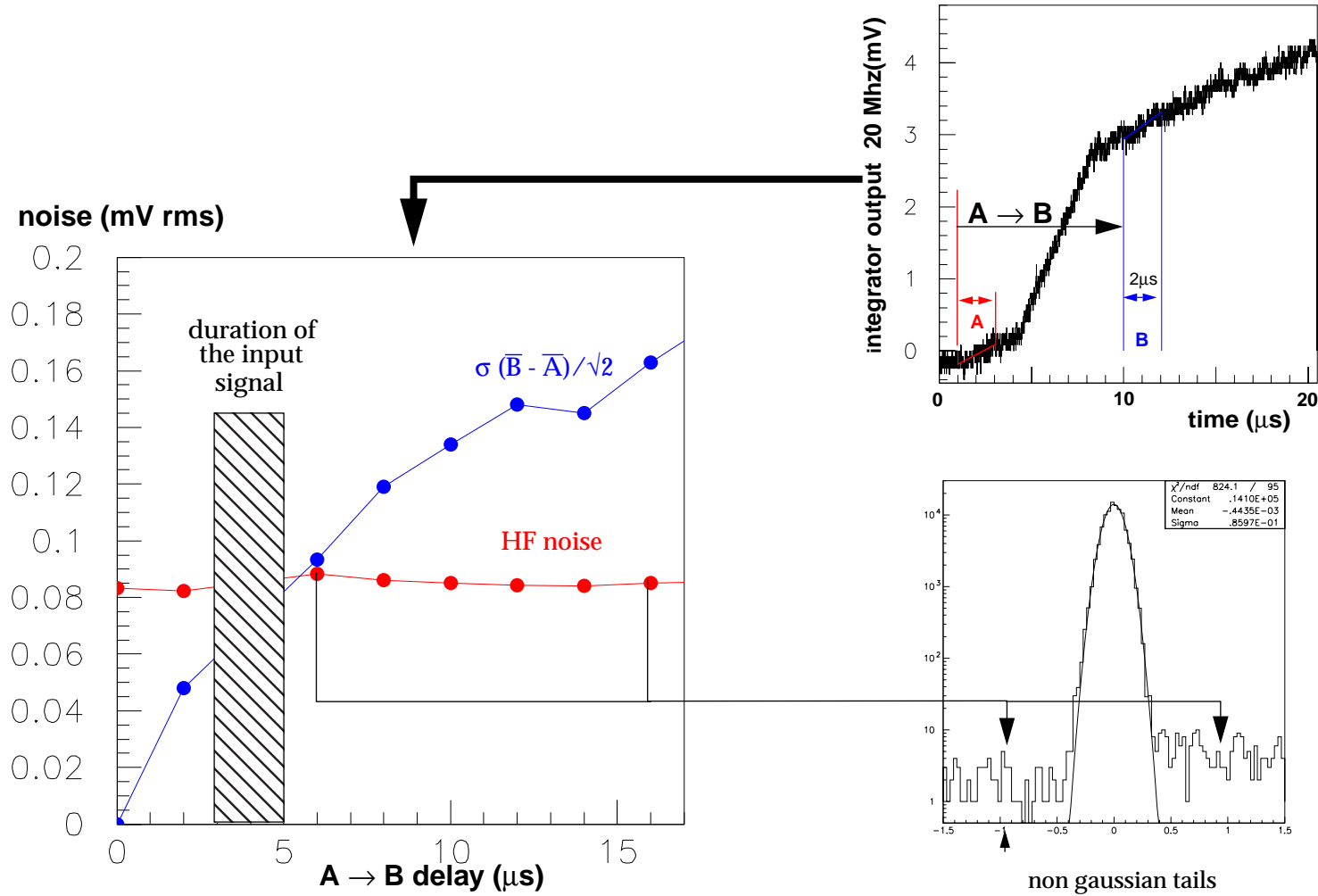


### PROBLEMS

- Baseline modulation by reset →

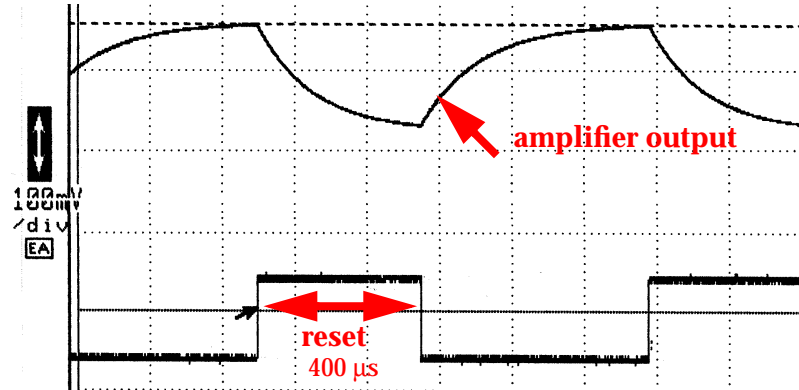

- transients on edges (amplifier out) →

 

- unstability of cds assembly (amp+int)

- etc...

NOT YET REPRODUCED BY ELECTRONIC SIMULATION



## PLANS

### **Analytic approach:**

- simulate the problems previously mentioned
- study of transients and timing constraints due to each switch, one at a time
- time constraints coming from the interaction between two clocks

### **System approach:**

- optimization of the time diagram
- optimization of the gain chain
- completion of our chain (CCD -CDS -digitizer)
- comparison with other (simpler?) analog chains

## CONCLUSION

*(please take first the positive aspect of each following statement)*

- Electronic noise seems a factor x2 above simulation (itself a factor x2 above CCD output). If this hypothesis is verified, it leads to a waste of ADC range *(all what can reasonably be predicted works well)*
- Our CDS prototype is at the top of the complexity scale. It might be difficult to understand all the problems only by signal analysis joined to electronic simulation *(they did pretty well with this complex circuit on the first try)*
- It is necessary to integrate all these elements in order to design a realistic analog chain for SNAP. In particular multiple gains would have a profound impact on this chain. A global perspective is important for us to focus our tests on real issues *(easier to simplify rather than the contrary)*