

Tens Picosenconds Digital ASIC
Time To Digital Converter for
Physics Experiments

stefano russo

Outline

- Why a time measure?
- Different TDCs
- The TEMPO TDC
- A first version @ 180nm
- The final chip @ 90nm

Why a time measure?

Time To Digital Converters (TDC) are widely used in many different fields



Physics experiments

- Time Of Flight
- Positron Emission Tomography (PET)
- Laser applications

...

Applied Electronics

- All digital frequency synthesis
- GFSK transceivers (frequency modulators)
- On chip test structures

...

All Digital TDC


Many different schemes to implement a TDC
(both analogic and digital)

Digital Scheme

- More performances on Available Technologies
- Easy to port design in different tech
- Performances scale almost linearly with tech

How to design a TDC

 To have a good resolution on a wide dynamic range a synchronous counter and asynchronous fine interpolator are realized




The fine measure

There are many different schemes to design the fine interpolator



Vernier Based

 The time interval is compared to a fixed time scale (like a caliper)




Direct Measure

The time interval is measured in terms of a fixed quantity (like a meter)


Vernier Based design examples

$\tau_2 \neq \tau_1$

 


$TLtH \neq THtL$

Resolution is
 $|\tau_2 - \tau_1|$

 

Direct Measure design

 


Resolution = t_{inv}

Which inverter?

In a direct measure scheme the inverter design is the key element to achieve a good resolution

CMOS inverter (static)

 


The inverter delay optimization is a tradeoff between:

- MOS dimensions
- parasitic C
- rise fall time

Which inverter?

NORA inverter (dynamic)


N type Inverter

 

The inverter needs a precharge signal (PRE) to be activated.

The output is valid after the signal EVAL


P type Inverter

 


NORA Logic

pros & cons

N type Inverter

 

P type Inverter

 

PRO


- speed (Eval parasites are not on the signal path)
- $TH2L \neq TL2H$

CONs


- Many signals
- $TH2L \neq TL2H$

NORA vs. CMOS

 
To evaluate the performances a comparative simulations was performed @ 180nm



NORA is
34%
Faster
than
CMOS

 


The TEMPO scheme

 


- High resolution
- Reduced dead time
- Low power

 Inverters in the fine interpolator are designed using NORA logic





The TEMPO scheme

 

A first chip @ 180nm (UMC)

  To validate our scheme a first version was realized




Full custom
design for
delay lines

TDC1 measure the
time between START
& Stop

TDC2 measure a
clock period
(calibration)

A first chip @ 180nm


Experimental Results

 


Resolution = 41 ps on 18 μ s range

A first chip @ 180nm

Experimental Results

 





Max Differential Non
Linearity
0.35 LSB

 

Max Integral Non
Linearity
0.75 LSB

A first chip @ 180nm


Experimental Results

    

Single shot precision histograms


A first chip @ 180nm

Experimental Results



 


Single shot precision temperature dependence

NORA vs. CMOS @ 90nm


 


NORA is
29%
Faster
than
CMOS

   

The TEMPO Differential scheme

  
The delay element compute two differential outputs.



The output is stabilized by the latch and acquired by a Strong Arm FF

A second chip @ 90nm (UMC)

 In the second chip the differential scheme was implemented



TDC1 measure the time between START & Stop


TDC2 measure a clock period (calibration)

Full custom design for delay lines


Measured resolution 25 ps over 10.6 μ s

A second chip @ 90nm

Experimental Results

 

Max Differential Non
Linearity
0.35 LSB

 

Max Integral Non
Linearity
0.65 LSB

Experimental Results Summary

Technology	Resolution	Range	Area	Power	INL	DNL
180nm	41ps	18 μ s	0.09mm	25mW	0.77LSB	0.35LSB
90nm	25ps	10.6 μ s	0.1mm	19mW	0.65LSB	0.35LSB